

EE4800/EE5880

Real Time Embedded Systems


Lessons 15 - 17

Memory Expansion

Overview

- Basic memory concepts
- Memory expansion
 - Linear and Paging techniques
- Guidelines
- Detailed memory expansion design techniques
 - Layout
 - Control signals
 - Timing issues

 Basic Memory Concepts capacity and control signals



Basic Memory Concepts

control signals

- /WE: write enable - when activated values on data lines are written to specified address
- /OE: output enable - data at specified location placed on data pins of memory chip, data lines connected to data bus using tristate outputs
- /CS: chip select - used to select a specific chip in memory array


Basic Memory Concepts

memory buses

- address bus

$2^{\text{addr lines}} = \text{addr locations}$

- data bus
- control bus

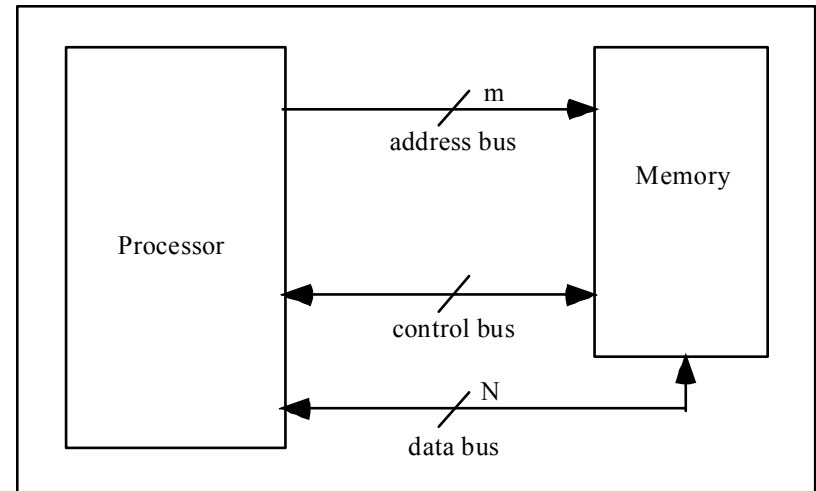

Basic Memory Concepts

RAM vs ROM

- RAM


- read/write
- volatile
- faster access time
- variants
 - SRAM
 - DRAM
- applications
 - variables
 - dynamic memory allocation
 - heaps, stacks

- ROM

- read only
- non-volatile
- slower
- variants
 - ROM, PROM, EPROM, EEPROM (byte-addressable, FLASH)
- applications
 - programs
 - constants, codes, etc.

Basic Memory Concepts

memory map

 

Memory Expansion

- Linear vs Paging
- Guidelines:
 - Unique address for each location
 - Data bus connected properly to all memory chips
 - Control lines routed to individual memory chips
 - Control signal timing are compatible between 68HC12 and external memory chips
 - External memory chips electrically compatible with 68HC12


Memory Expansion Overview

- Memory layout design
 - Based on Dr. Jerry Cupal's techniques
- Control signals
 - 68HC12
 - external memory components
- Timing compatibility

Memory Expansion layout design


- From system requirements determine amount of external devices needed
- Draw the desired memory table and design the address decoding and control logic
- Draw the schematic of the circuit
- Verify the design

Memory Expansion expanding memory length

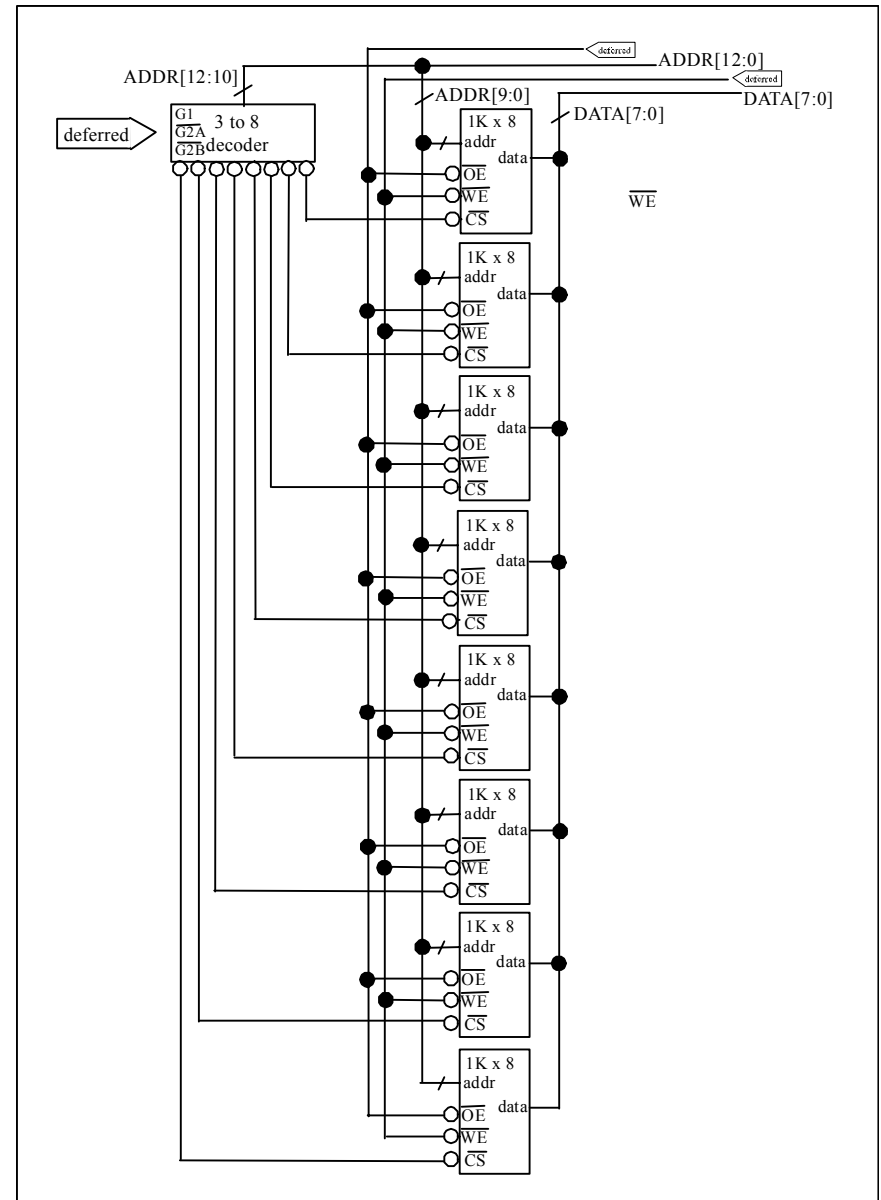


Memory Expansion

expanding memory width

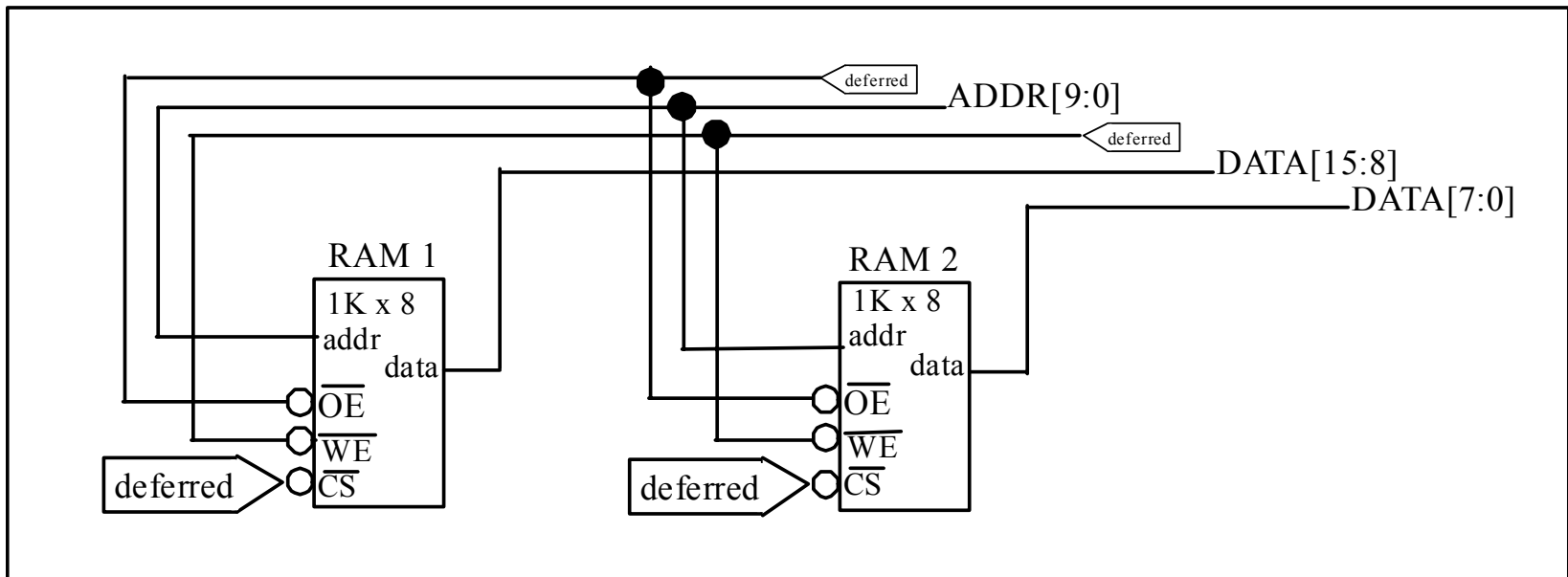

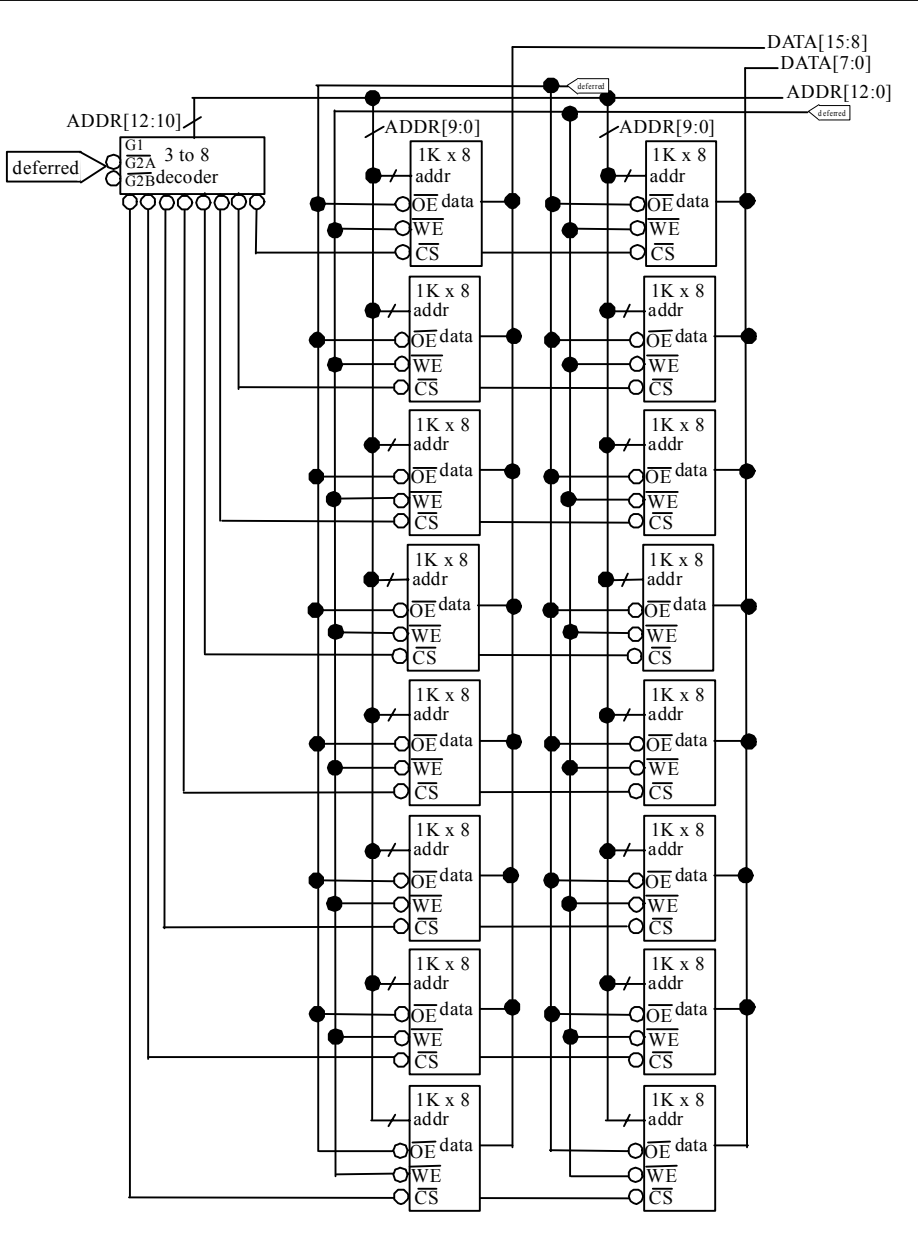Memory Expansion expanding memory length and width




Memory Expansion memory table

| Device | A ₁₅ | A ₁₄ | A ₁₃ | A ₁₂ | A ₁₁ | A ₁₀ | A ₉ | A ₈ | A ₇ | A ₆ | A ₅ | A ₄ | A ₃ | A ₂ | A ₁ | A ₀ | Useable Locations |
|--------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|-------------------|
| RAM0 | 0 | 0 | 1 | 0 | 0 | 0 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$2000 - \$23FF |
| RAM1 | 0 | 0 | 1 | 0 | 0 | 1 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$2400 - \$27FF |
| RAM2 | 0 | 0 | 1 | 0 | 1 | 0 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$2800 - \$2BFF |
| RAM3 | 0 | 0 | 1 | 0 | 1 | 1 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$2C00 - \$2FFF |
| RAM4 | 0 | 0 | 1 | 1 | 0 | 0 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$3000 - \$33FF |
| RAM5 | 0 | 0 | 1 | 1 | 0 | 1 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$3400 - \$37FF |
| RAM6 | 0 | 0 | 1 | 1 | 1 | 0 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$3800 - \$3BFF |
| RAM7 | 0 | 0 | 1 | 1 | 1 | 1 | ● | ● | ● | ● | ● | ● | ● | ● | ● | ● | \$3C00 - \$3FFF |

Memory Expansion control signals

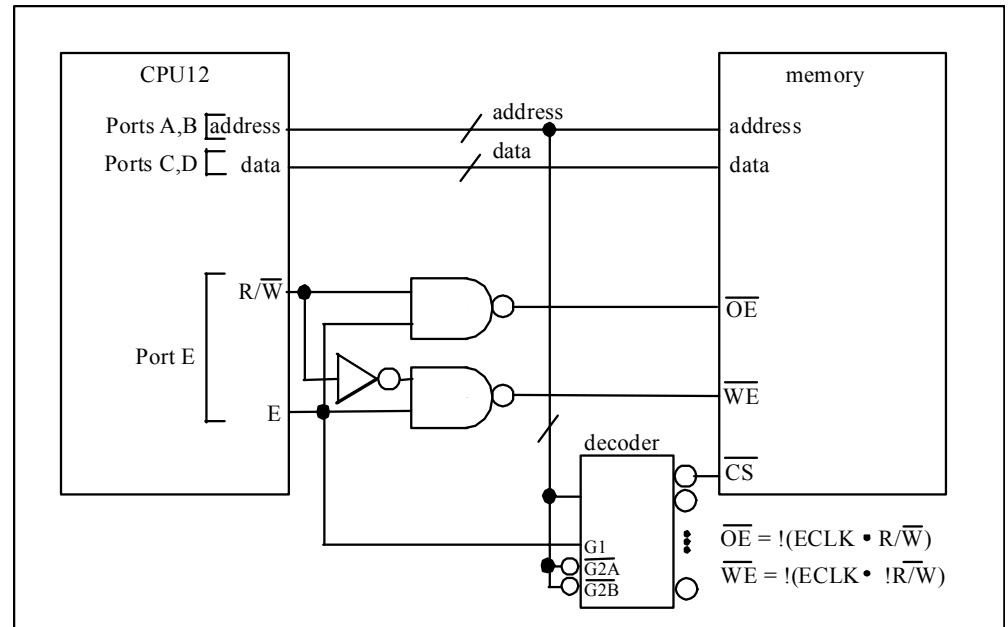- 68HC12 control signals
 - ECLK: basic bus clock
 - $\overline{R/W}$: indicates data direction
- Memory chips control signals
 - \overline{WE} : write enable
 - \overline{OE} : output enable
 - \overline{CS} : chip select



Memory Expansion timing analysis overview

- Must analyze timing compatibility between processor and memory
- Must analyze:
 - RAM
 - read cycle
 - write cycle
 - ROM
 - read cycle

Memory Expansion

timing analysis - RAM read cycle

- A valid address is placed on address lines ADDR[15:0]
- Control signals are issued by 68HC12
 - ECLK and $\overline{R/\overline{W}}$
- Provides control inputs to memory components
 - $\overline{/CS}$ and $\overline{/OE}$
- Data are read from the external memory by 68HC12

Memory Expansion

timing analysis - nonmultiplexd expansion bus timing

| Num | Characteristic ^{(1), (2)} | Delay | Symbol | 5 MHz | | Unit |
|-----|---|-------|------------|-------|-----|------|
| | | | | Min | Max | |
| | Frequency of operation (E-clock frequency) | — | f_0 | dc | 8.0 | MHz |
| 1 | Cycle time $t_{cyc} = 1/f_0$ | | t_{cyc} | 125 | — | ns |
| 2 | Pulse width, E low $PW_{EL} = t_{cyc}/2 + \text{delay}$ | -2 | PW_{EL} | 60 | — | ns |
| 3 | Pulse width, E high ⁽³⁾ $PW_{EH} = t_{cyc}/2 + \text{delay}$ | -2 | PW_{EH} | 60 | — | ns |
| 5 | Address delay time $t_{AD} = t_{cyc}/4 + \text{delay}$ | 29 | t_{AD} | — | 60 | ns |
| 6 | Address hold time | — | t_{AH} | 20 | — | ns |
| 7 | Address valid time to E rise $t_{AV} = PW_{EL} - t_{AD}$ | — | t_{AV} | 0 | — | ns |
| 11 | Read data setup time | — | t_{DSR} | 30 | — | ns |
| 12 | Read data hold time | — | t_{DHR} | 0 | — | ns |
| 13 | Write data delay time $t_{DDW} = t_{cyc}/4 + \text{delay}$ | 25 | t_{DDW} | — | 46 | ns |
| 14 | Write data hold time | — | t_{DHW} | 20 | — | ns |
| 15 | Write data setup time ⁽³⁾ $t_{DSW} = PW_{EH} - t_{DDW}$ | — | t_{DSW} | 30 | — | ns |
| 16 | Read/write delay time $t_{RWD} = t_{cyc}/4 + \text{delay}$ | 18 | t_{RWD} | — | 49 | ns |
| 17 | Read/write valid time to E rise $t_{RWV} = PW_{EL} - t_{RWD}$ | — | t_{RWV} | 20 | — | ns |
| 18 | Read/write hold time | — | t_{RWH} | 20 | — | ns |
| 19 | Low strobe delay time $t_{LSD} = t_{cyc}/4 + \text{delay}$ | 18 | t_{LSD} | — | 49 | ns |
| 20 | Low strobe valid time to E rise $t_{LSV} = PW_{EL} - t_{LSD}$ | — | t_{LSV} | 11 | — | ns |
| 21 | Low strobe hold time | — | t_{LSH} | 20 | — | ns |
| 22 | Address access time ⁽³⁾ $t_{ACCA} = t_{cyc} - t_{AD} - t_{DSR}$ | — | t_{ACCA} | — | 35 | ns |
| 23 | Access time from E rise ⁽³⁾ $t_{ACCE} = PW_{EH} - t_{DSR}$ | — | t_{ACCE} | — | 30 | ns |
| 26 | Chip-select delay time $t_{CSD} = t_{cyc}/4 + \text{delay}$ | 29 | t_{CSD} | — | 60 | ns |
| 27 | Chip-select access time ⁽³⁾ $t_{ACCS} = t_{cyc} - t_{CSD} - t_{DSR}$ | — | t_{ACCS} | — | — | ns |
| 28 | Chip-select hold time | — | t_{CSH} | — | — | ns |
| 29 | Chip-select negated time $t_{CSN} = t_{cyc}/4 + \text{delay}$ | 5 | t_{CSN} | — | — | ns |

1. $V_{DD} = 5.0 \text{ Vdc} \pm 10\%$, $V_{SS} = 0 \text{ Vdc}$, $T_A = T_L$ to T_H , unless otherwise noted.

2. All timings are calculated for normal port drives.


3. This characteristic is affected by clock stretch.

Add $N \times t_{cyc}$ where $N = 0, 1, 2,$ or 3 , depending on the number of clock stretches.

Figure 8.15 Nonmultiplexed expansion bus timing definitions. (Figure used with permission of Motorola, Incorporated.)

Memory Expansion

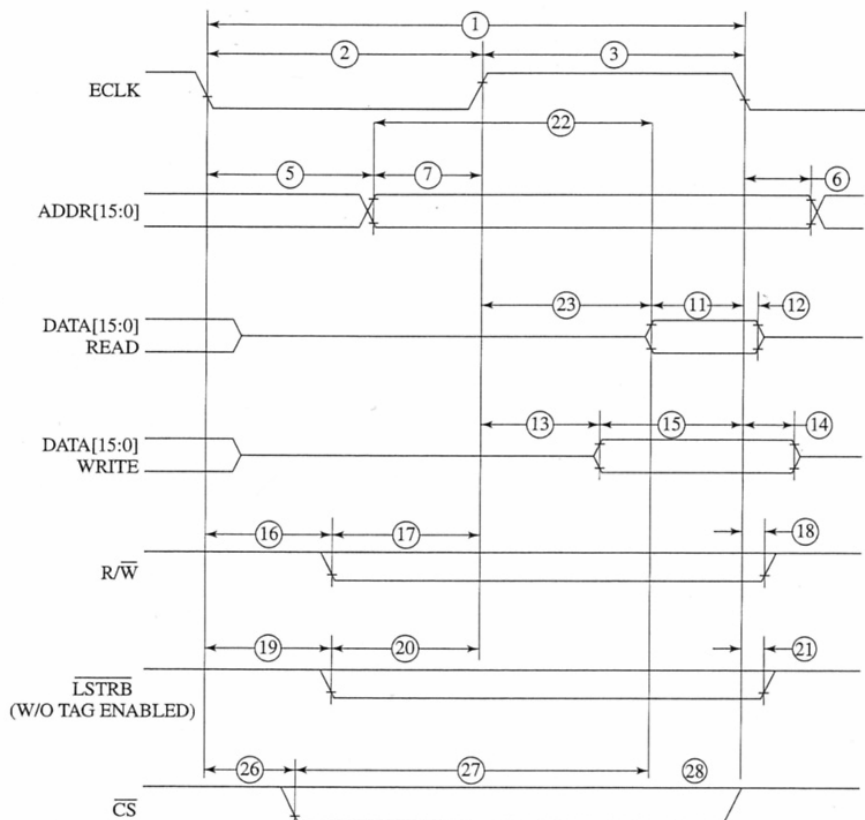timing analysis - nonmultiplexd expansion bus timing




Note: Measurement points shown are 20% and 70% of V_{DD} .

Figure 8.16 Nonmultiplexed expansion bus timing diagram. (Figure used with permission of Motorola, Incorporated.)

Memory Expansion

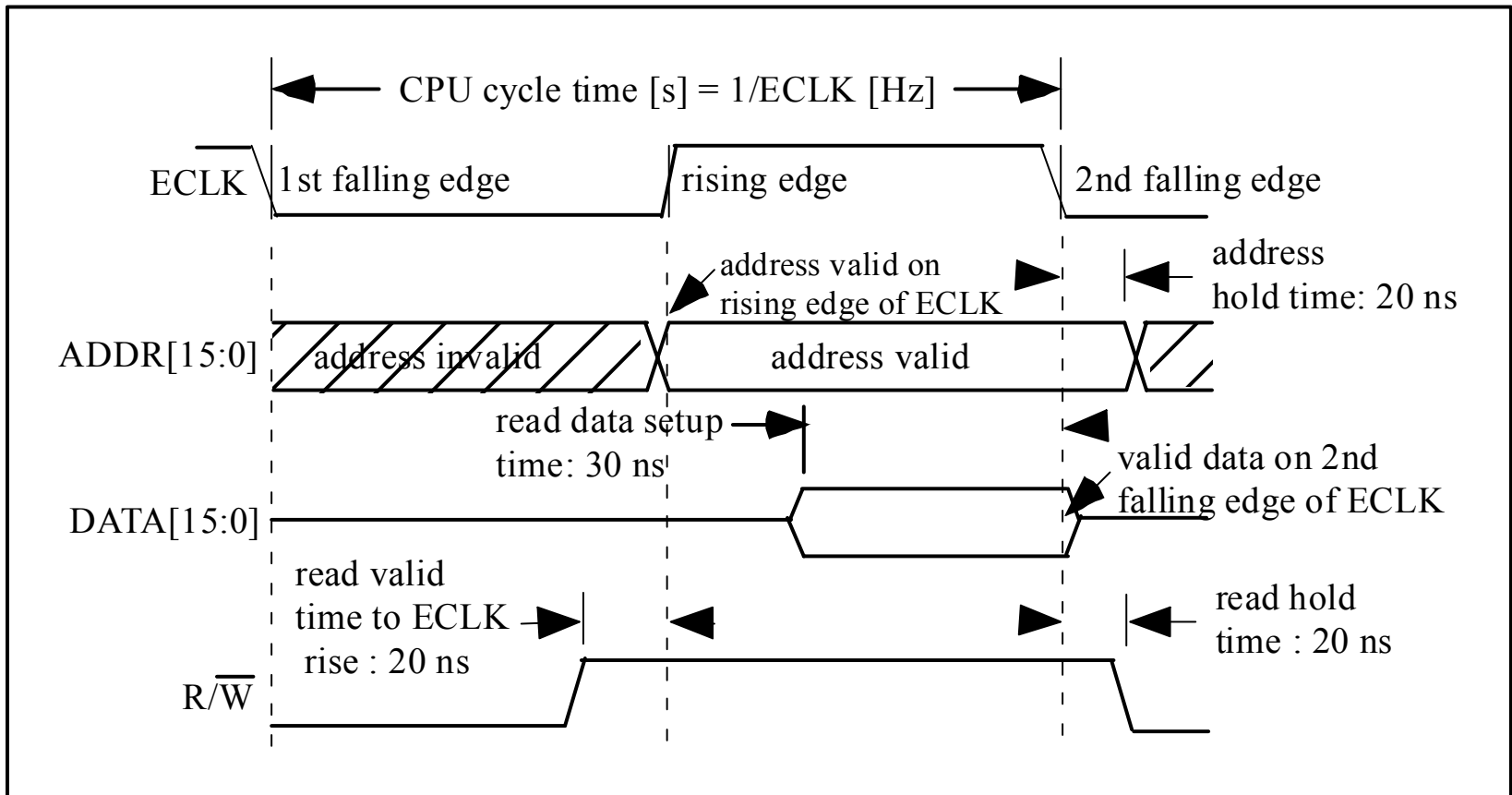
timing analysis - simplified timing diagram



Memory Expansion

timing analysis - timing signals

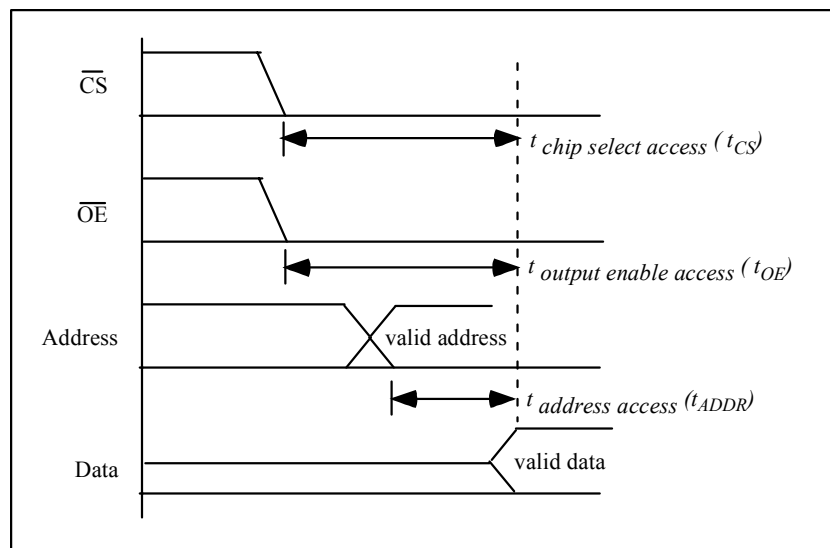- Chip select access time (t_{CS})
- Address access time (t_{ADDR})
- Output enable access time (t_{OE})



Memory Expansion

four key questions

- **Q1:** How soon can valid data be provided by the SRAM memory chip after a chip select signal is provided by the 68HC12 under worst-case conditions?
- **Q2:** How soon can valid data be provided by the memory chip after a valid address is provided under worst-case conditions?
- **Q3:** How soon can valid data be provided to the 68HC12 once the memory chip has received a valid output enable signal?
- **Q4:** Final analysis - choose worst case situation