

EE4800-03

Embedded Systems Design

Lessons 11-12

Input/Output Interfacing Concepts

Overview - Input/Output Interfacing


- Voltage and current characteristics
- Loading
- Input devices
- Output devices
- Fanout
- Interfacing to other devices

Voltage and Current Characteristics

- V_{OH} : lowest guaranteed output voltage for logic high
- V_{OL} : highest guaranteed output voltage for logic low
- I_{OH} : the output current for logic high (- current source)
- I_{OL} : the output current for logic low (+ current sink)
- V_{IH} : lowest input voltage guaranteed as logic high
- V_{IL} : highest input voltage guaranteed as logic low
- I_{IH} : the input current for logic high (+ current sink)
- I_{IL} : the input current for logic low (- source sink)


Voltage and Current Characteristics for “HC” CMOS Devices

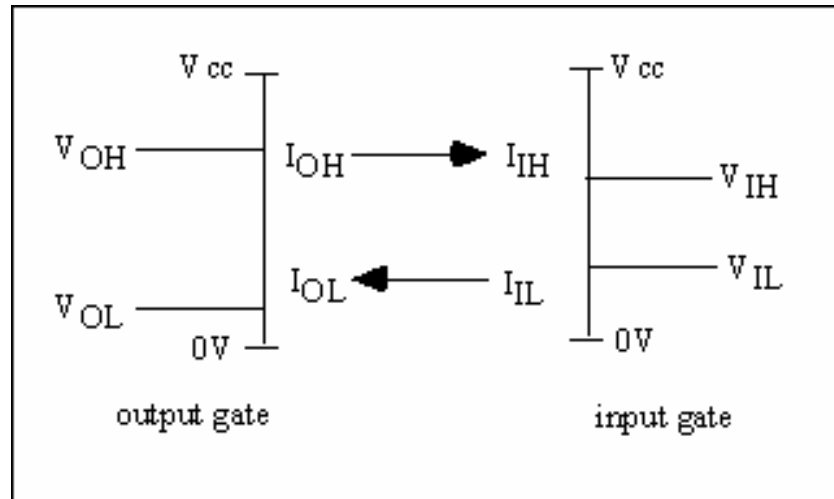- V_{OH} : 4.2 volts
- V_{OL} : 0.4 volts
- I_{OH} : -0.8 mA
- I_{OL} : 1.6 mA
- V_{IH} : 3.5 volts
- V_{IL} : 1.0 volt
- I_{IH} : 10 μ A
- I_{IL} : -10 μ A
- Fanout example




Loading

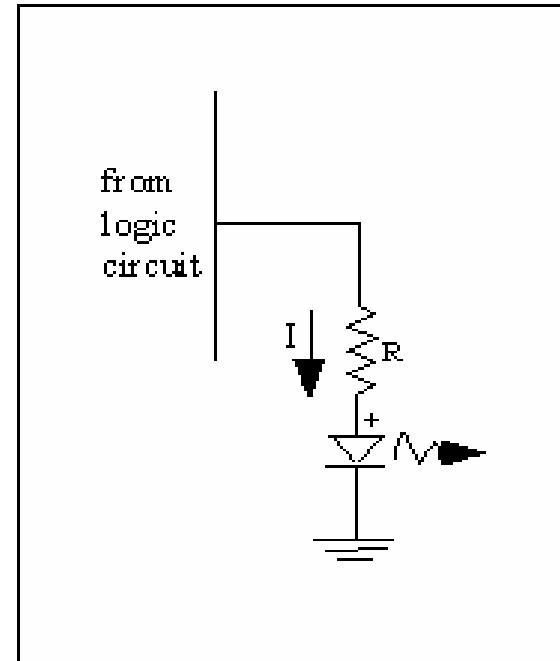- Reference Fig 5.2
- In logic high condition, I_{OH} values greater than -0.8 mA will cause V_{OH} to decrease
- In logic low condition, I_{OL} greater than 1.6 mA will cause V_{OL} to increase
- Both may cause faulty logic levels in downstream systems



Input/Output Devices

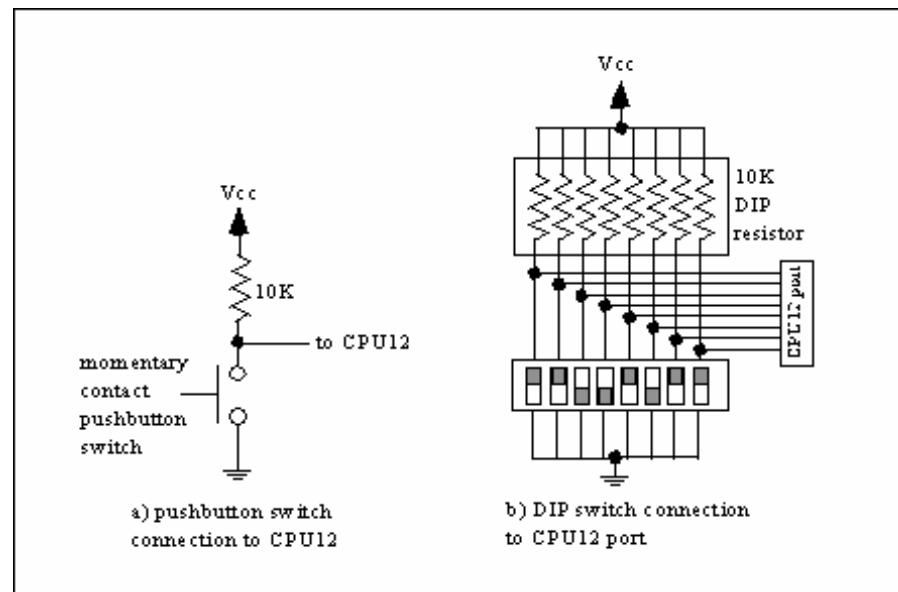- Momentary pushbutton
 - interrupt
- DIP switches
 - configuration
- Keypad
 - data entry
- LEDs
 - status entries
- 7 segment display
 - data display




Switch debouncing

- Switches are mechanical devices
- When switch is flipped it makes/breaks contacts multiple times - called bouncing
 - processor fast enough to see each bounce as independent input
 - debounce with hardware, software, or HW/SW techniques

Switch debouncing - techniques -

- Hardware

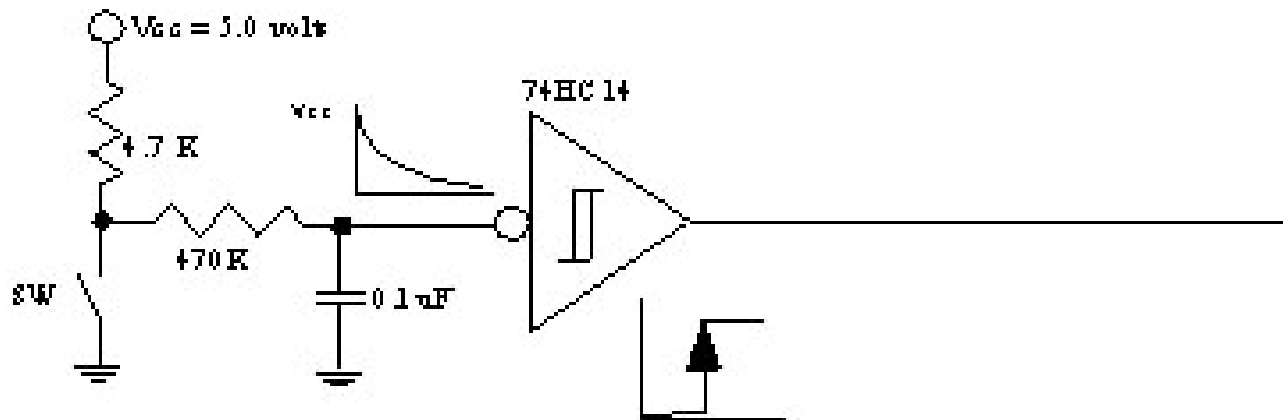


- Software

- after first transition provide 25-50 ms delay


Terminating Unused Inputs

- Input impedance is very high on unused input pins
- If not connected, the input can oscillate or float to midsupply level
- Oscillation can couple noise to power supply
- Terminate unused input pins by pulling up (or down) via a resistor -- 4.7 Kohm


Keypad

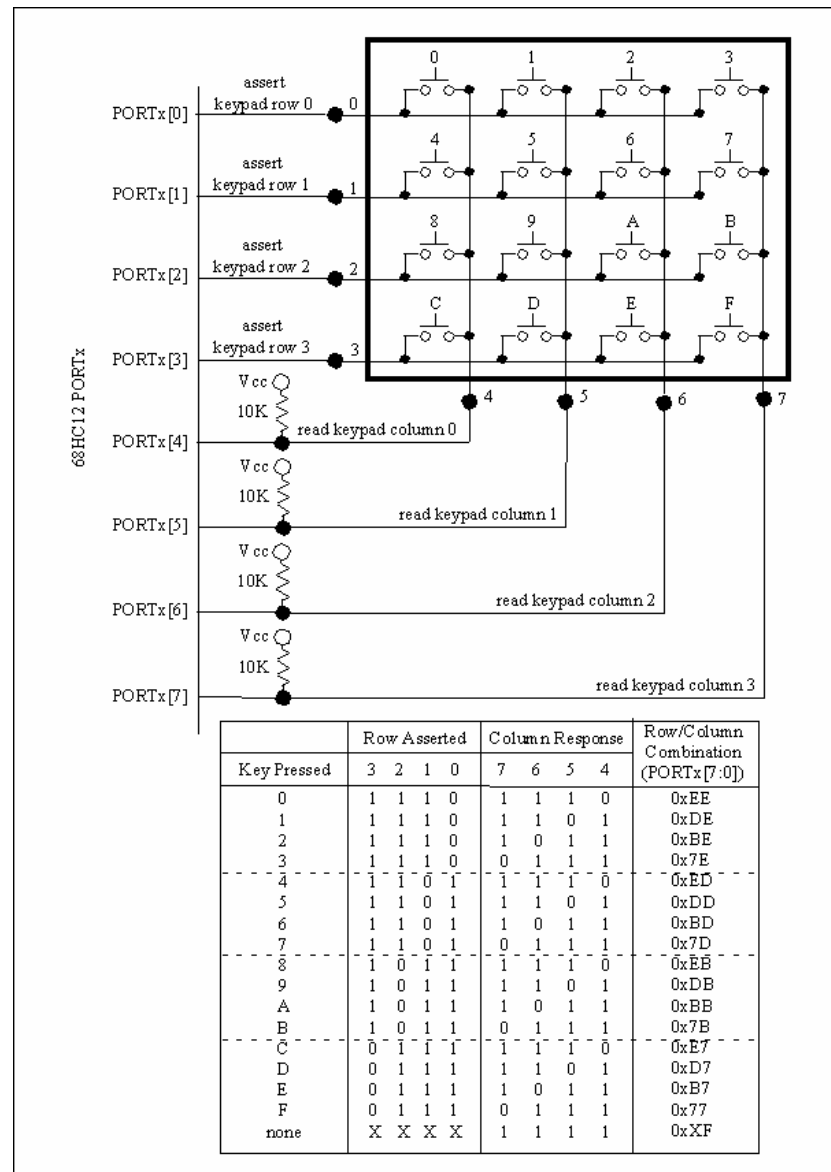

Indicators

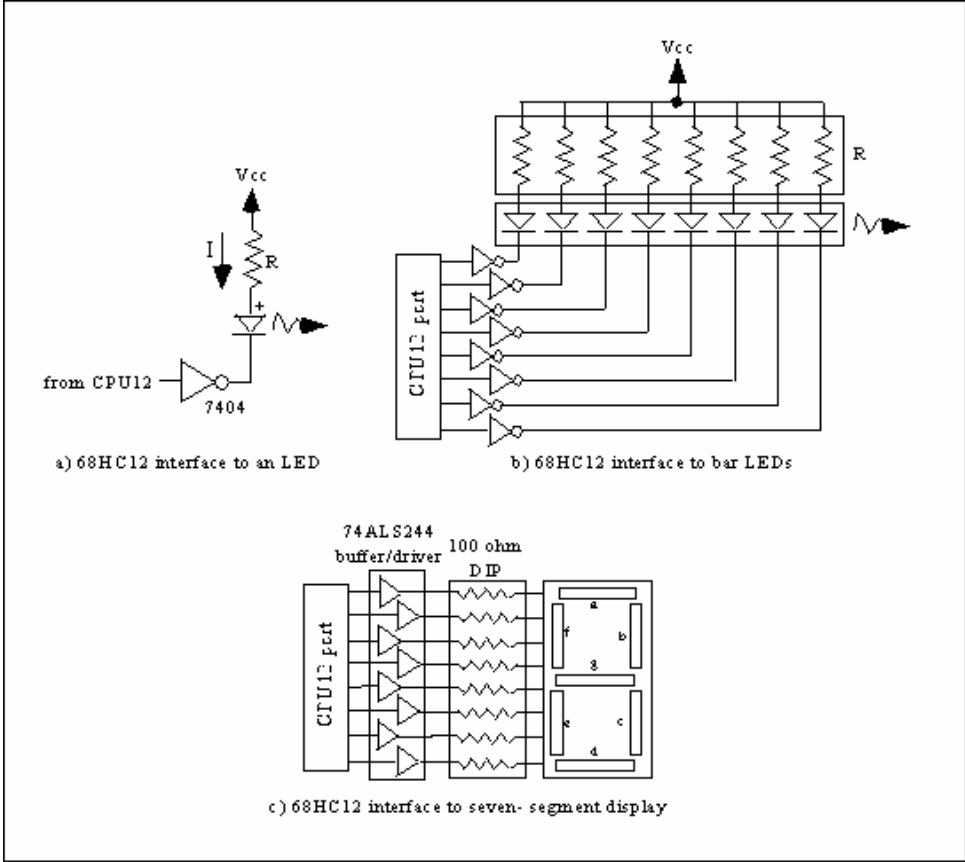


Tri-state Logic

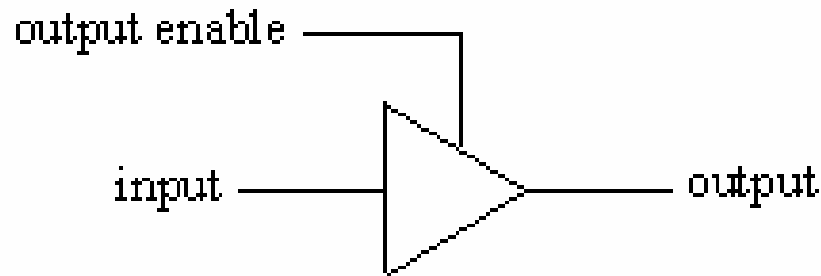


output enable	input	output
L	L	High-Z
L	H	High-Z
H	L	L
H	H	H

Tri-state indicator circuit

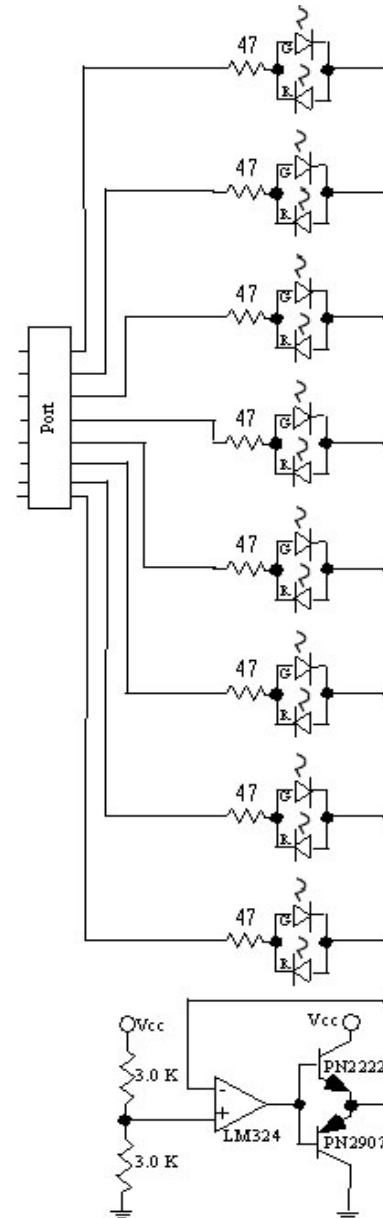
- Tri-state indicator:
 - Green: logic high
 - Red: logic low
 - None: high impedance



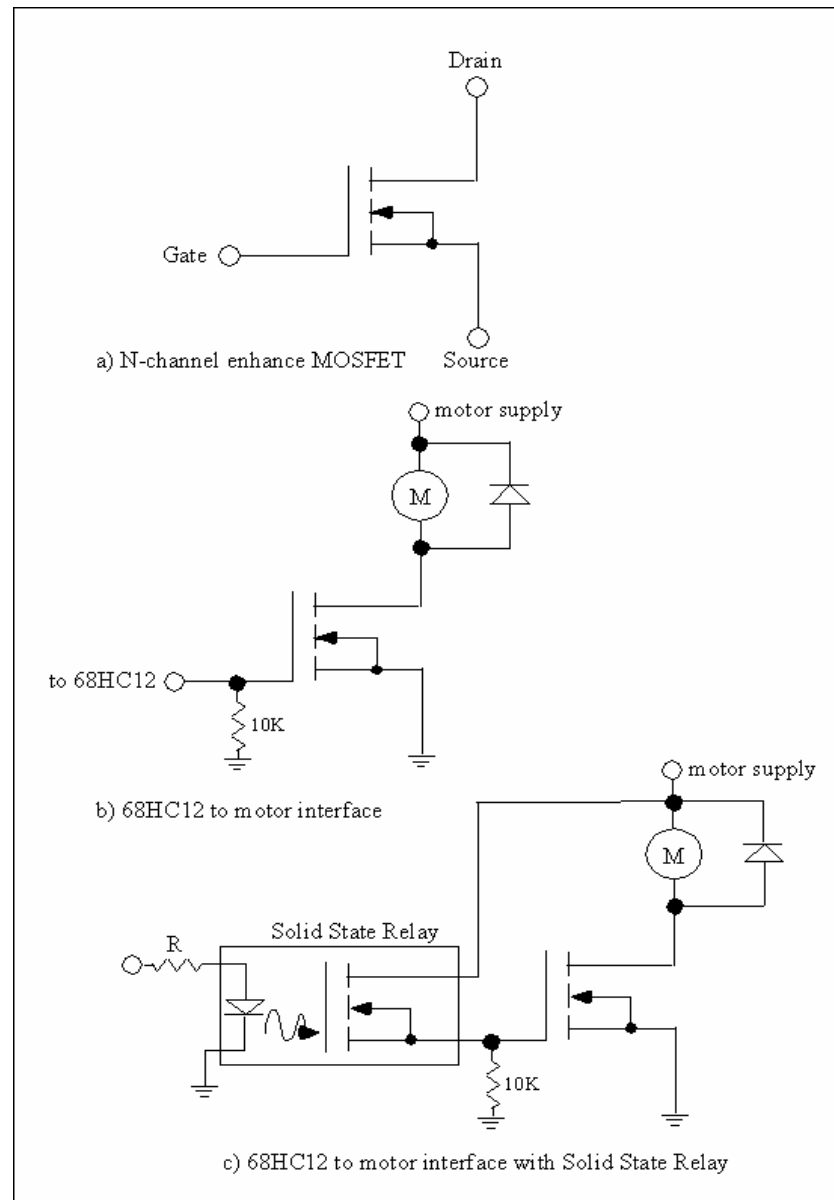Interfacing to other Devices - Motor Control




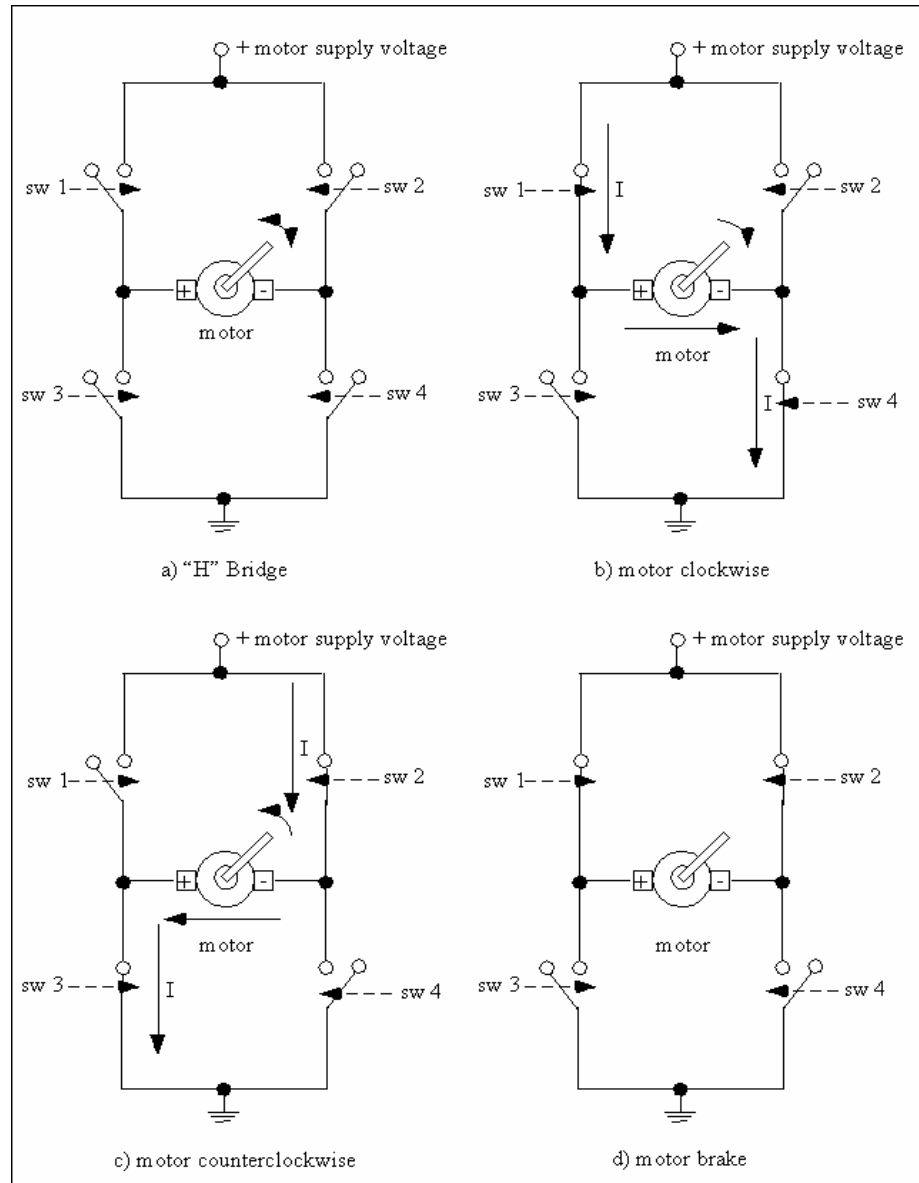Interfacing to Other Devices - Bi-directional motor control




Interfacing to Other Devices

- Bi-directional motor control

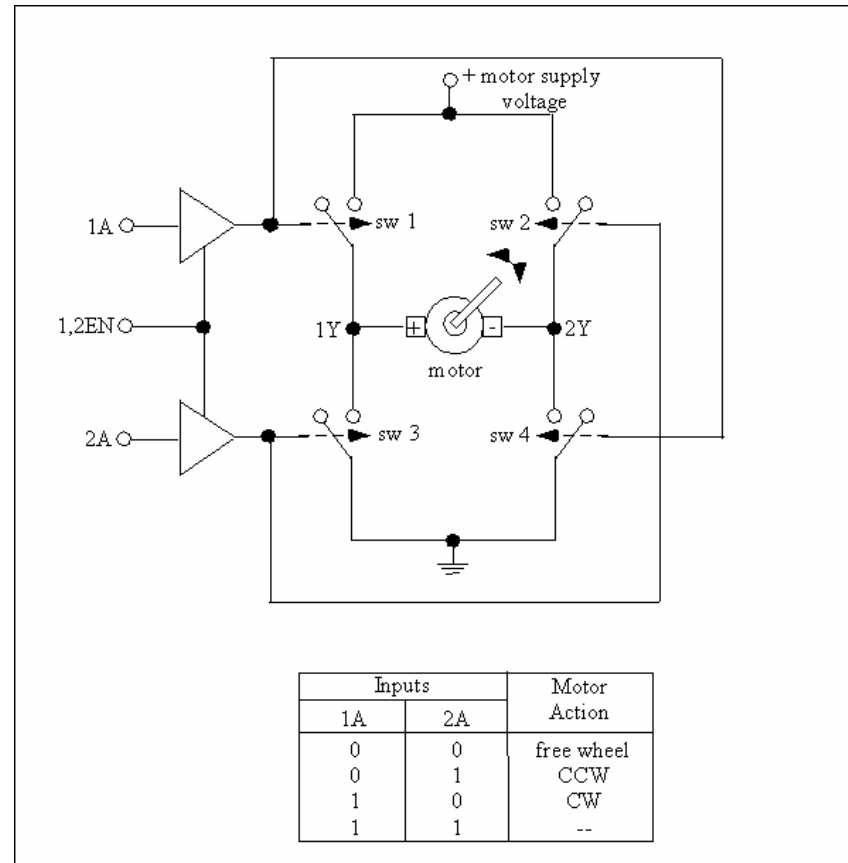


Interfacing to Other Devices

- RS-232 Interface

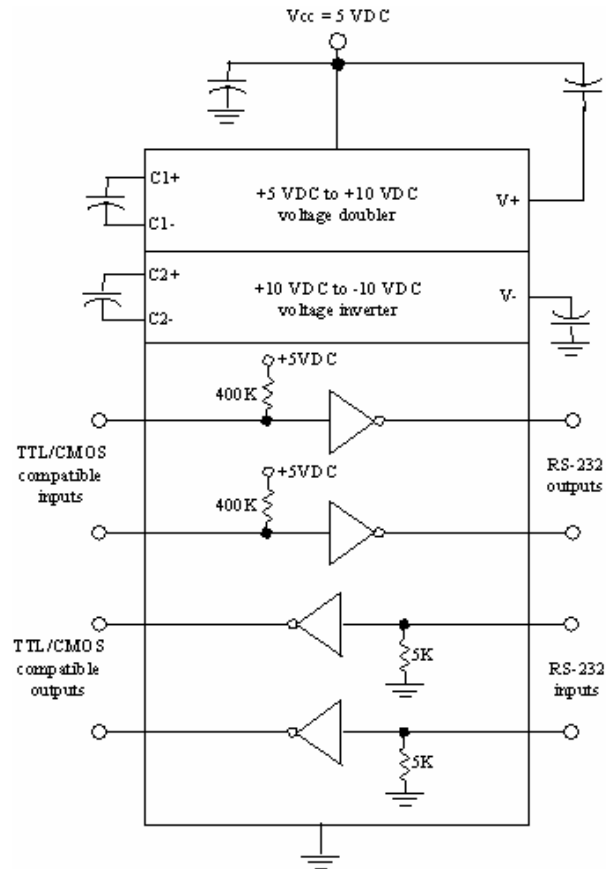

Interfacing to Other Devices

- Transducer Interface Design

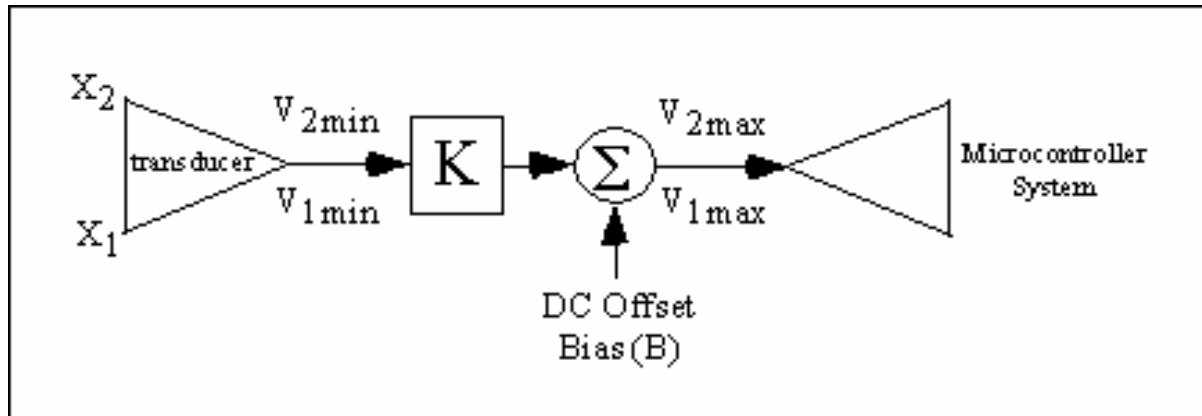

$$V_{2max} = V_{2min} * K + B$$

$$V_{1max} = V_{1min} * K + B$$